

## Test on the resistance and resistors

Complete the following test, taking the previous results into account:

Here are several test questions. Say which of the following options is true for each sentence:

1. Total resistance equivalent to various series is always:
  - a) Greater than the highest of them
  - b) Less than the lowest of them
  - c) Greater than the sum of them
  - d) Depends on the value of the resistances
2. Total resistance equivalent to various parallel resistances is always:
  - a) Greater than the highest of them
  - b) Less than the lowest of them
  - c) Greater than the sum of them
  - d) Depends on the value of the resistances
3. Total resistance equivalent to various parallel or series is always:
  - a) Greater than the highest of them
  - b) Less than the lowest of them
  - c) Greater than the sum of them
  - d) Depends on the value of the resistances
4. For two series of the same value, total resistance is:
  - a) Double its value
  - b) Half its value
  - c) Double the sum of its value
  - d) Half the opposite of its value
5. For two parallel of the same value, total resistance is:
  - a) Double its value
  - b) Half its value
  - c) Double the sum of its value
  - d) Half the opposite of its value
6. What can be added to a series to ensure that the new total resistance is nearly the same as the original – in other words, to ensure that it is not affected much?
  - a) A very high resistor (10 times greater than the first one)
  - b) A very low resistor (10 times less than the first one)
  - c) Nothing should be added because this always affects it, however little this may be

- d) Any resistor
7. What can be added in parallel to ensure that the new total resistance is nearly the same as the original – in other words, to ensure that it is not affected much?
- a) A very high resistor (10 times greater than the first one)
  - b) A very low resistor (10 times less than the first one)
  - c) Nothing should be added because this always affects it, however little this may be
  - d) Any resistance
8. Using 10K and 1K resistors, how should you connect them in order to obtain a total resistance of around 1.9K?
- a) By connecting two 1K resistors in series
  - b) By connecting 1K resistor and 10K resistor in parallel, and 1K resistor in series to these
  - c) By connecting 1K resistor and 10K resistor in series, and 1K resistor in parallel to these
  - d) This cannot be done
9. Using 10K and 1K resistors, how should you connect them in order to obtain a total resistor of more or less 10.9K?
- a) By connecting two 1K resistors in series
  - b) By connecting 1K resistor and 10K resistor in parallel, and 10K resistor in series to these
  - c) By connecting 1K resistor and 10K resistor in series, and 10K resistor in parallel to these
  - d) By connecting 1K resistor and 10K resistor in parallel, and 1K resistor in series to these
10. Using 10K and 1K resistances, how should you connect them in order to obtain a total resistance of more or less 1.5K?
- a) By connecting three 1K resistances in series
  - b) By connecting one 1K resistance and another 1K resistance in parallel, and one 10K resistance in series to these
  - c) By connecting one 1K resistance and another 1K resistance in series, and one 1K resistance in parallel to these
  - d) By connecting one 1K resistance and another 10K resistance in parallel, and one 1K resistance in series to these