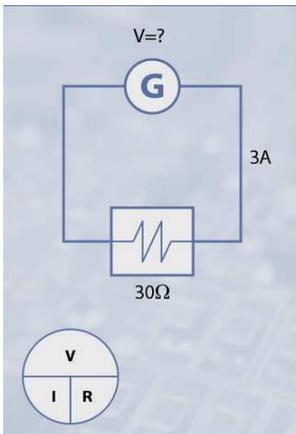


Exercises


Take a look at the following figures and choose correct answer on the questions provided.

Exercise 1: Based on the Ohm's Law concept what voltage is in the circuit?




- 90 volts
- 9 volts
- 0.1 volts
- 0.9 volts

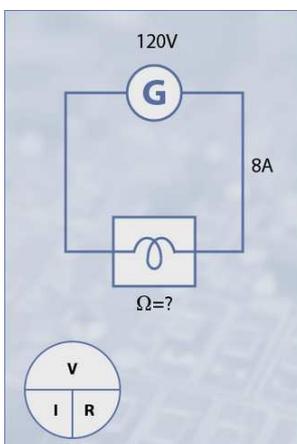Exercise 2: Based on the Ohm's Law concept what resistance is in circuit?



- .0666...
- 15
- 960

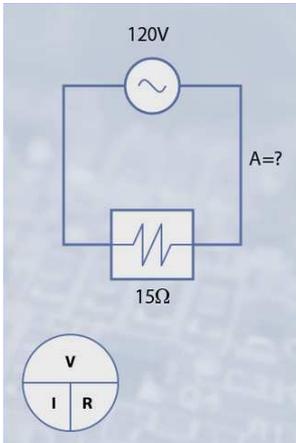Exercise 3: Based on the Ohm's Law concept what current is in the circuit?



The circuit has amperes.